



國立勤益科技大學

National Chin-Yi University of Technology

**Sedra/Smith**

**Microelectronic Circuits 6/E**




**Chapter 2: Operational Amplifiers**

## 【Outline】

- 2.1 The Ideal OP Amp
- 2.2 The Inverting Configuration
- 2.3 The Noninverting Configuration
- 2.4 Difference Amplifiers
- 2.5 Integrators and Differentiators
- 2.6 DC Imperfections
- 2.7 Effect of Finite Open-Loop Gain and Bandwidth on  
Circuit Performance
- 2.8 Large-Signal Operation of Op Amp



## 2-1 The ideal op amp

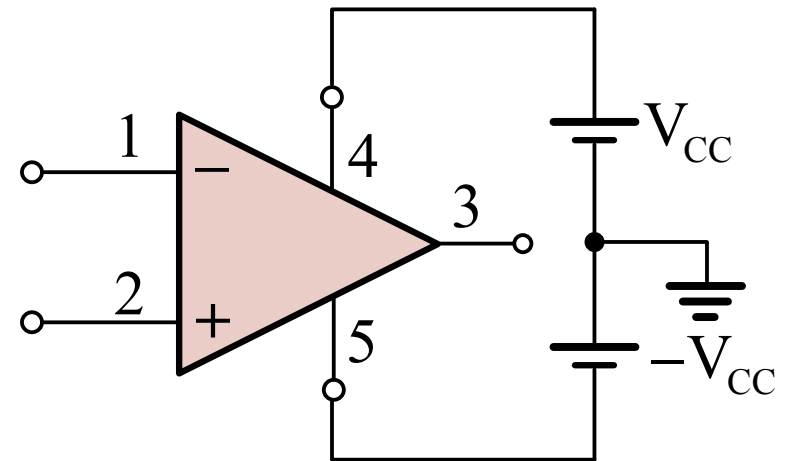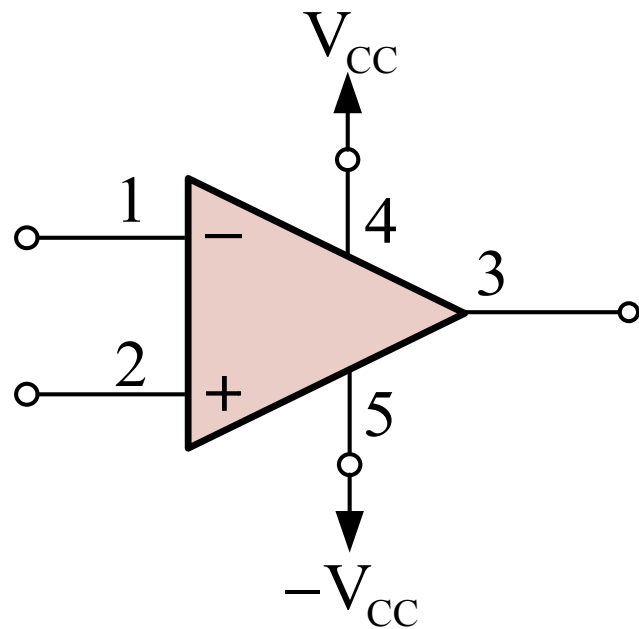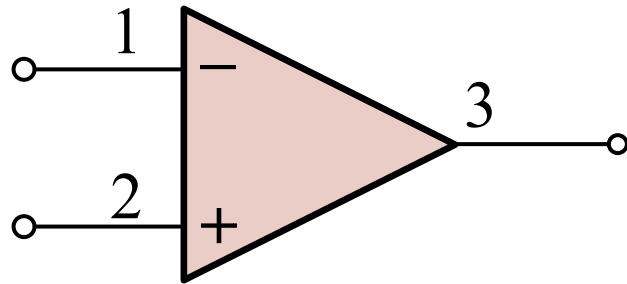

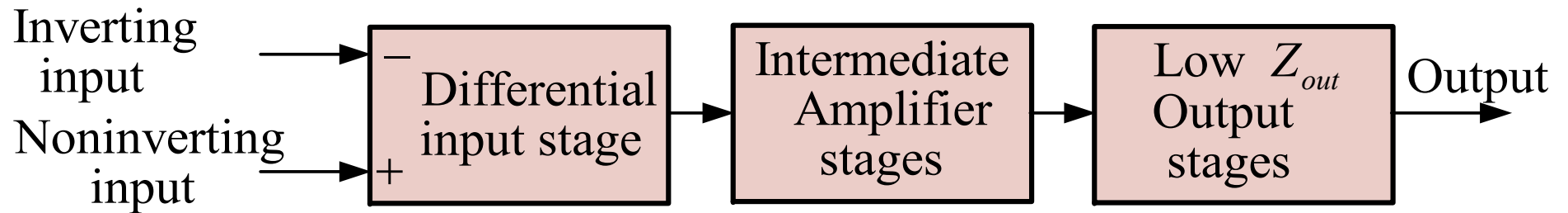



Figure 1. Block diagram of an operational amplifier

The properties associated with an ideal Amplifier are:

1. infinite voltage gain (  $A_v \rightarrow \infty$  )
2. Infinite input impedance (  $Z_{in} \rightarrow \infty$  )
3. Zero output impedance(  $Z_{out} \rightarrow 0$  )
4. Output voltage  $V_{out} = 0$  when input voltages  $V_1 = V_2$
5. Infinite bandwidth ( no delay of the signal through the amplifier)


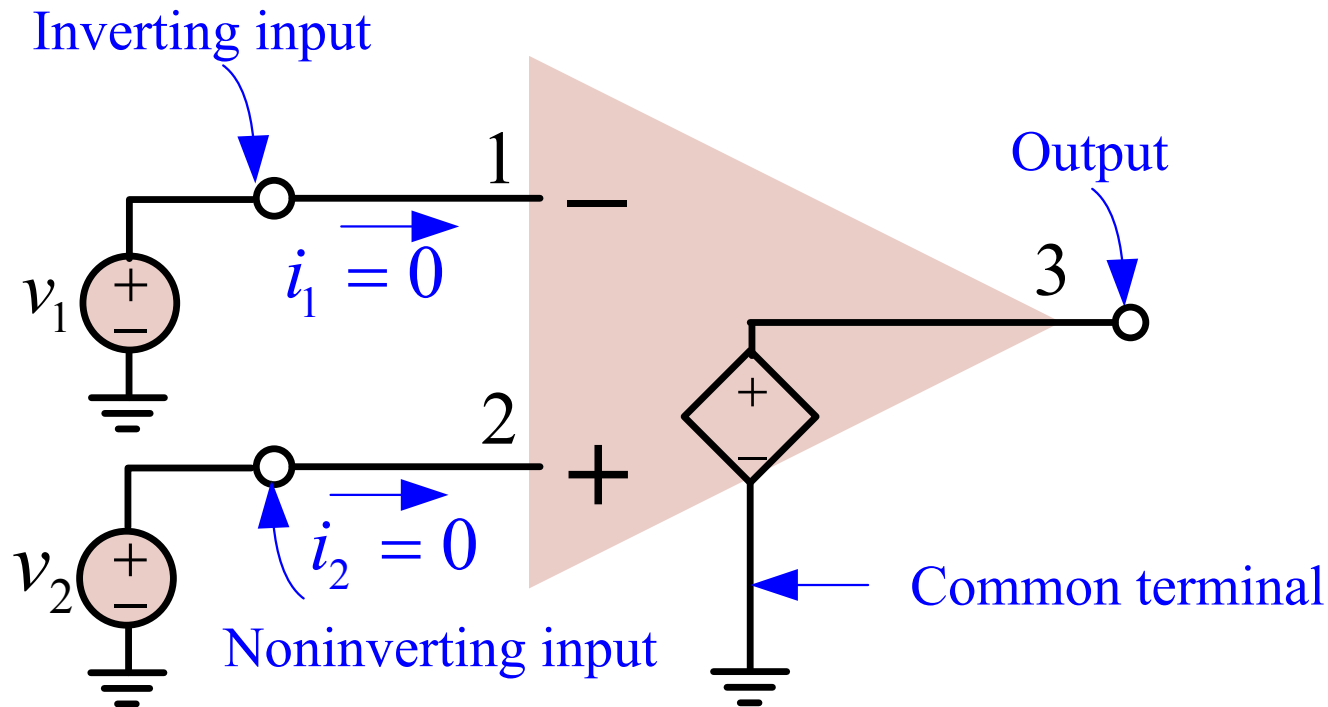
## 2.1.2 Function and Characteristics of the ideal Op Amp




(virtual short circuit:  $v_i = 0, I_i = 0, R_{in} = \infty$ )



## Some Specifications

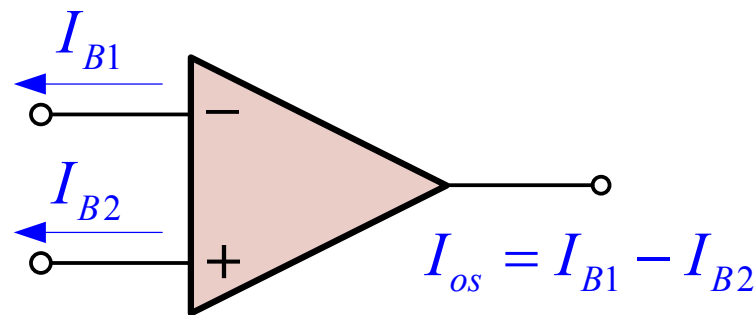1. Open loop gain (  $A_{ol}$  ): Usually several thousand.
2. Input offset voltage (  $V_{os}$  ): Small, usually a few millivolts.
3. Input offset current (  $I_{os}$  ): Usually between a few and several hundred nanoamps.



4. Input resistance (  $R_{in}$  ): Typically greater than one megohm, but it can be as high as several hundred megohms.
5. Output resistance (  $R_{out}$  ): Usually less than a few hundred ohms.
6. Slew rate (  $S$  ): The maximum rate of output voltage change given in volts per microsecond.

7. 
$$\text{CMRR} = \frac{A_d}{A_{cm}}$$



## 2.1.3 Differential and Common-Mode Signal


The difference input signal  $v_{id}$  :

$$v_{id} = v_2 - v_1$$



The Common-mode input signal  $v_{icm}$  :

$$v_{icm} = (v_2 + v_1) / 2$$
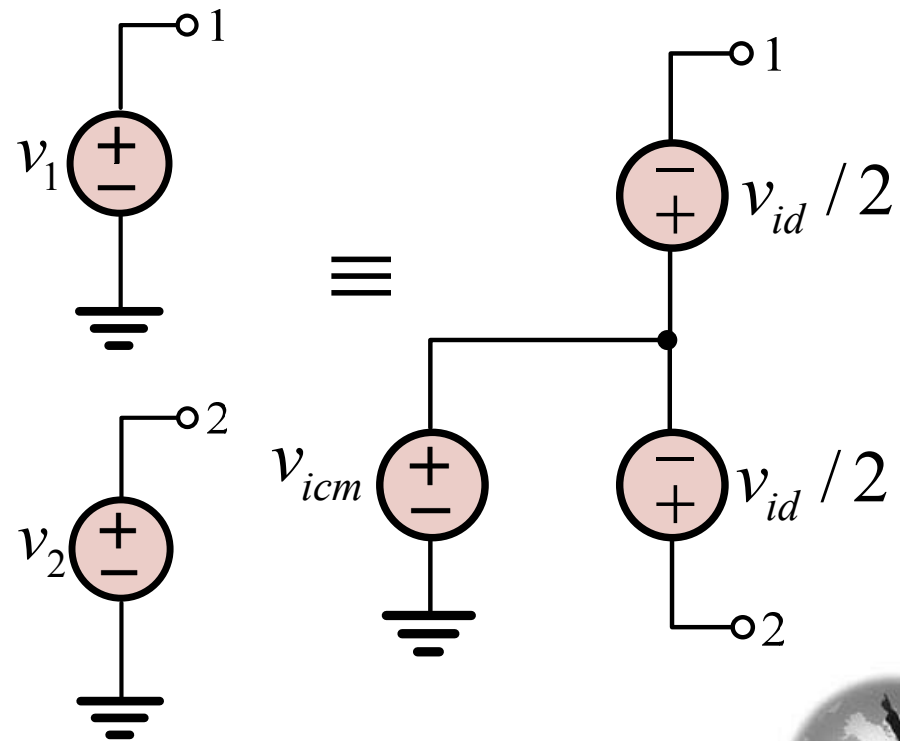
$$\Rightarrow \begin{cases} v_1 = v_{icm} - v_{id} / 2 \\ v_2 = v_{icm} + v_{id} / 2 \end{cases}$$



## 2.2 The inverting configuration

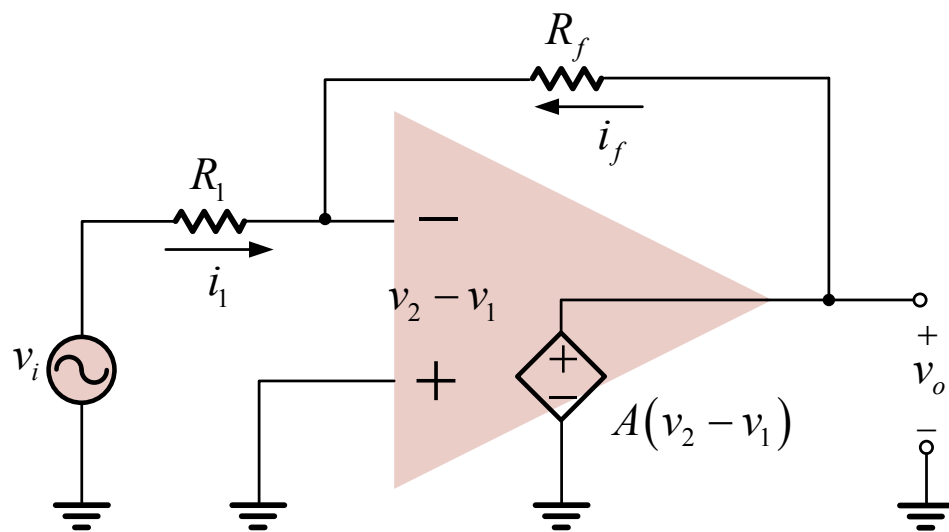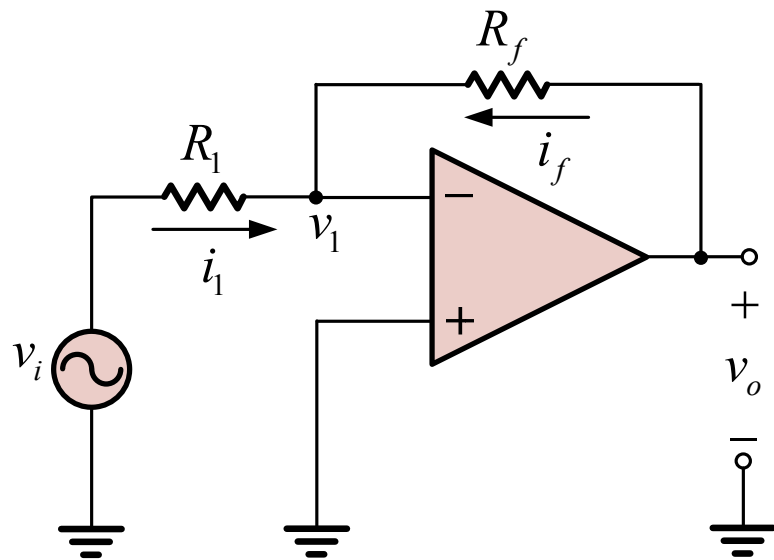

$$v_2 - v_1 = \frac{v_o}{A} = 0$$

(virtual short circuit:

$$v_i = 0, I_i = 0, R_{in} = \infty)$$

$$i_1 = \frac{v_i - v_1}{R_1} = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1}$$

$$v_o = v_1 + i_f R_f = v_1 - i_1 R_f$$


$$= 0 - \frac{v_i}{R_1} R_f$$

$$G = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$$





## 2.2.2 Effect of Finite Open-Loop Gain

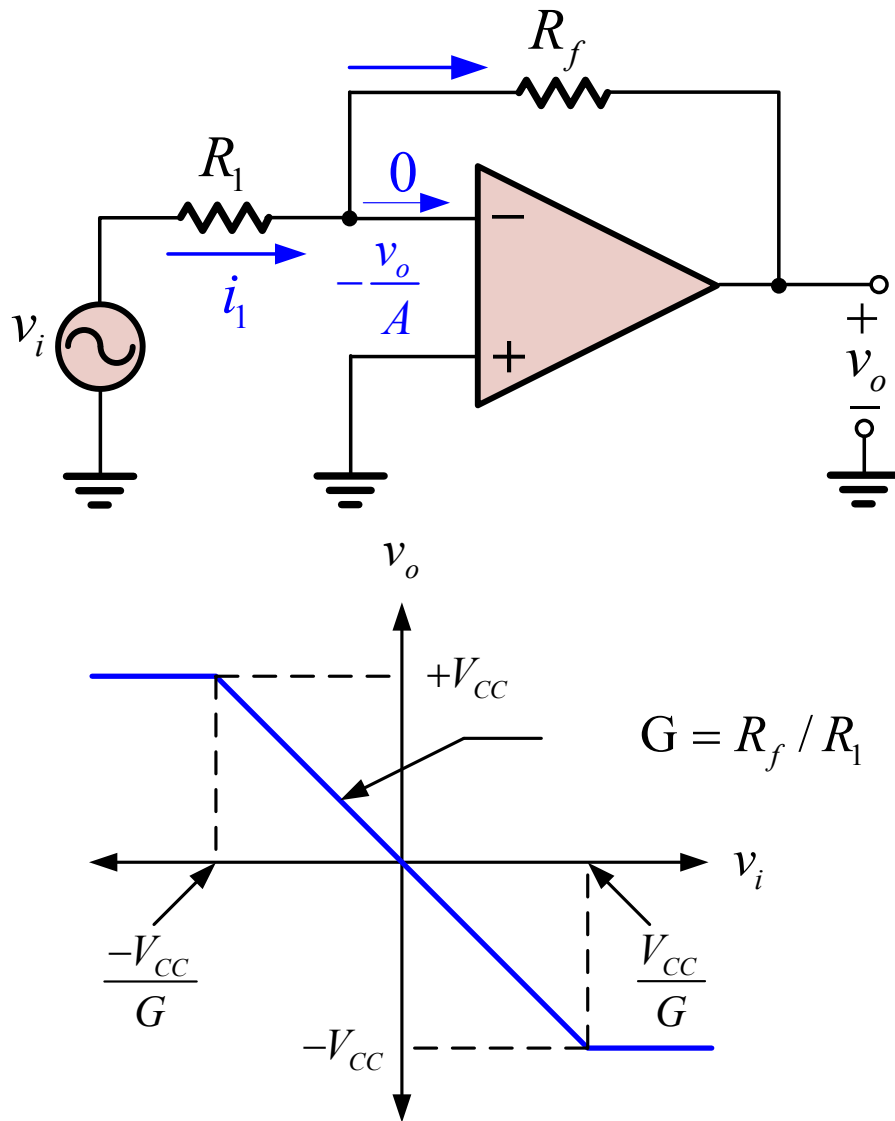

$$i_1 = \frac{v_i - (-v_o / A)}{R_1}$$

$$= \frac{v_i + v_o / A}{R_1}$$


$$v_o = -\frac{v_o}{A} - i_1 R_f$$

$$= -\frac{v_o}{A} - \left( \frac{v_i + v_o / A}{R_1} \right) R_f$$

$$G \equiv \frac{v_o}{v_i} = \frac{-R_f / R_1}{1 + (1 + R_f / R_1) / A} \quad (2.5)$$

when  $A \rightarrow \infty, G \rightarrow -R_f / R_1$

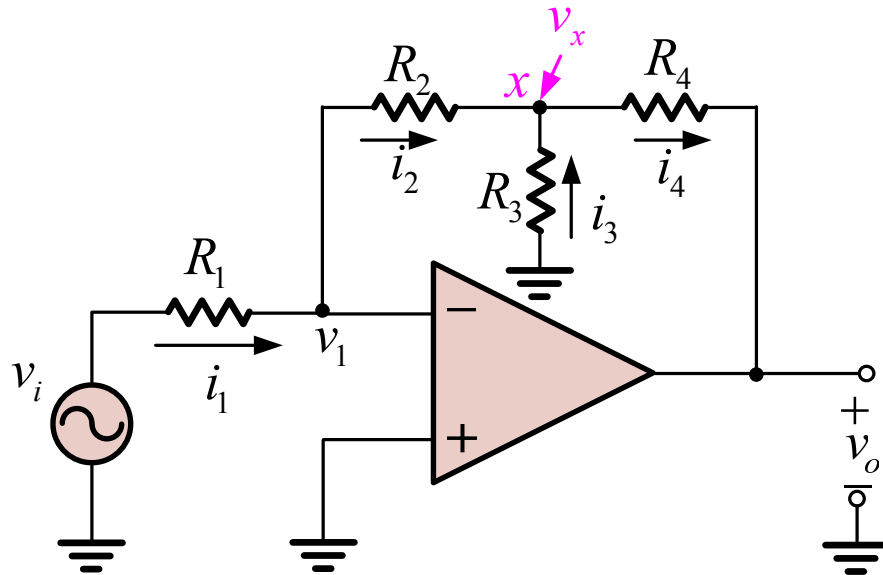**Example 2.2:** Assuming the op amp to be ideal, derive an expression for closed-loop gain  $v_o / v_i = ?$



**Solution**

$$v_i = \frac{-v_o}{A} = \frac{-v_o}{\infty} = 0 \text{ (virtual short)}$$

$$i_1 = -\frac{v_i - v_1}{R_1} = \frac{v_i}{R_1}$$

$$i_2 = i_1 = \frac{v_i}{R_1}$$

$$v_x = v_1 - i_2 R_2 = 0 - \left( \frac{v_i R_2}{R_1} \right)$$

$$= -v_i R_2 / R_1$$

$$i_3 = \frac{0 - v_x}{R_3} = \frac{R_2}{R_1 R_3} v_i$$

$$i_4 = i_2 + i_3 = \frac{v_i}{R_1} + \frac{R_2}{R_1 R_3} v_i$$


$$v_o = v_x - i_4 R_4$$

$$= -\frac{v_i}{R_1} R_2 - \left( \frac{v_i}{R_1} + \frac{R_2}{R_1 R_3} v_i \right) R_4$$

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_2} \frac{R_4}{R_3} \right)$$


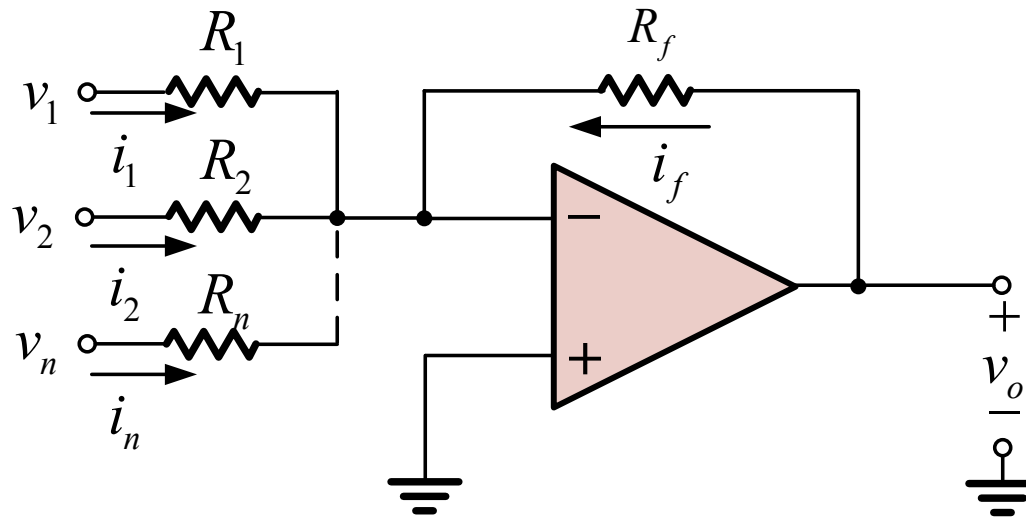
## 2.2.4 An Important Application – The Weighted Summer



$$i_1 = \frac{v_1}{R_1}, i_2 = \frac{v_2}{R_2}, I_n = \frac{v_n}{R_n}, \quad I_f = \frac{v_o}{R_f}$$



$$I_f = -(I_1 + I_2 + \dots + I_n) \quad \Rightarrow \quad \frac{v_o}{R_f} = -\left( \frac{v_1}{R_1} + \frac{v_2}{R_2} + \dots + \frac{v_n}{R_n} \right)$$

$$v_o = -\left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right) \quad (2.7)$$

If  $R_1 = R_2 = \dots = R_n = R_f$  Then  $v_o = -(v_1 + v_2 + \dots + v_n)$



## 2.3 The Noninverting Configuration

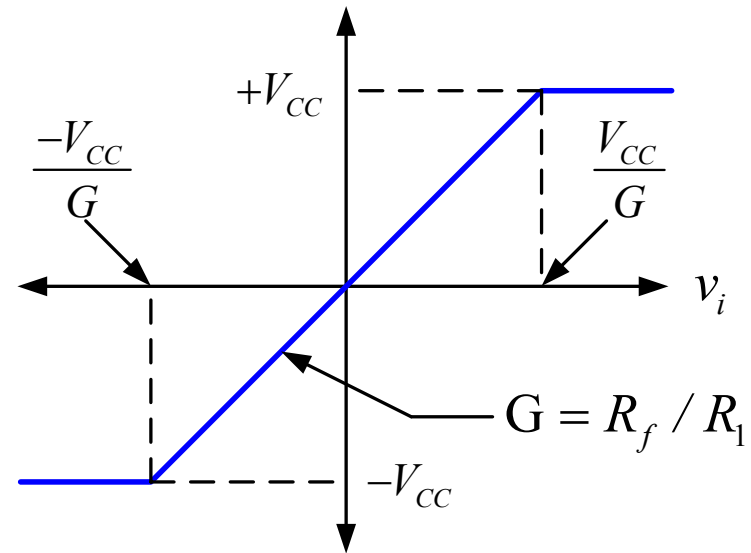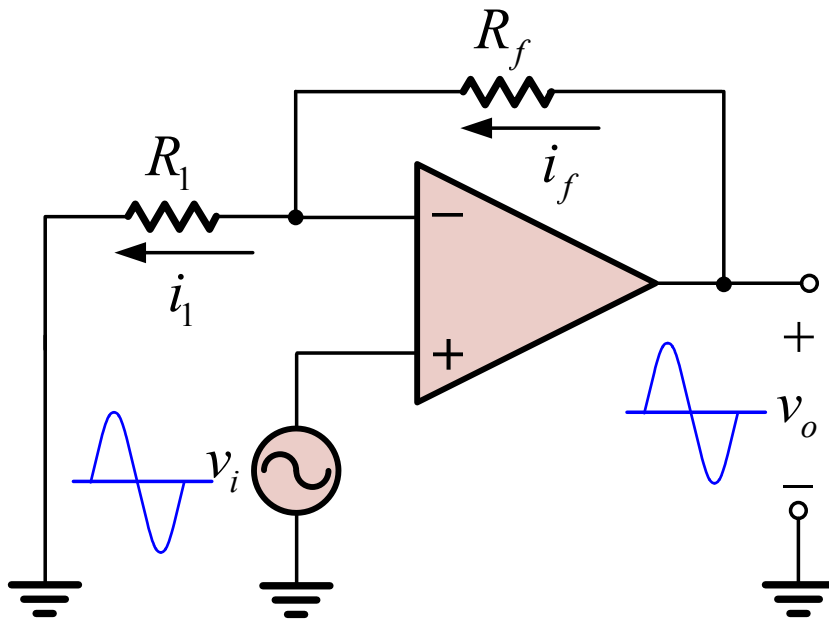

$$i_1 = \frac{v_i}{R_1}, \quad i_f = \frac{v_o - v_i}{R_f}$$

$$i_1 = i_f \Rightarrow \frac{v_i}{R_1} = \frac{v_o - v_i}{R_f}$$

$$\Rightarrow v_o = \left(1 + \frac{R_f}{R_1}\right)v_i$$



### 2.3.3 Effect of Finite Open-Loop Gain

$$v_- = v_i - (v_o / A)$$

$$i_1 = \frac{v_i - (v_o / A)}{R_1}, i_f = \frac{v_o - [v_i - (v_o / A)]}{R_f} = \frac{v_o - v_i + (v_o / A)}{R_f},$$

$$i_1 = i_f \Rightarrow \frac{v_i - (v_o / A)}{R_1} = \frac{v_o - v_i + (v_o / A)}{R_f}$$


$$v_i A(R_1 + R_f) = v_o [(1 + A)R_1 + R_f]$$

$$G \equiv \frac{v_o}{v_i} = \frac{1 + (R_f / R_1)}{1 + \frac{1 + (R_f / R_1)}{A}} \quad (2.11)$$

when  $A \rightarrow \infty, G \rightarrow 1 + (R_f / R_1)$




## 2.3.4 The Voltage Follower

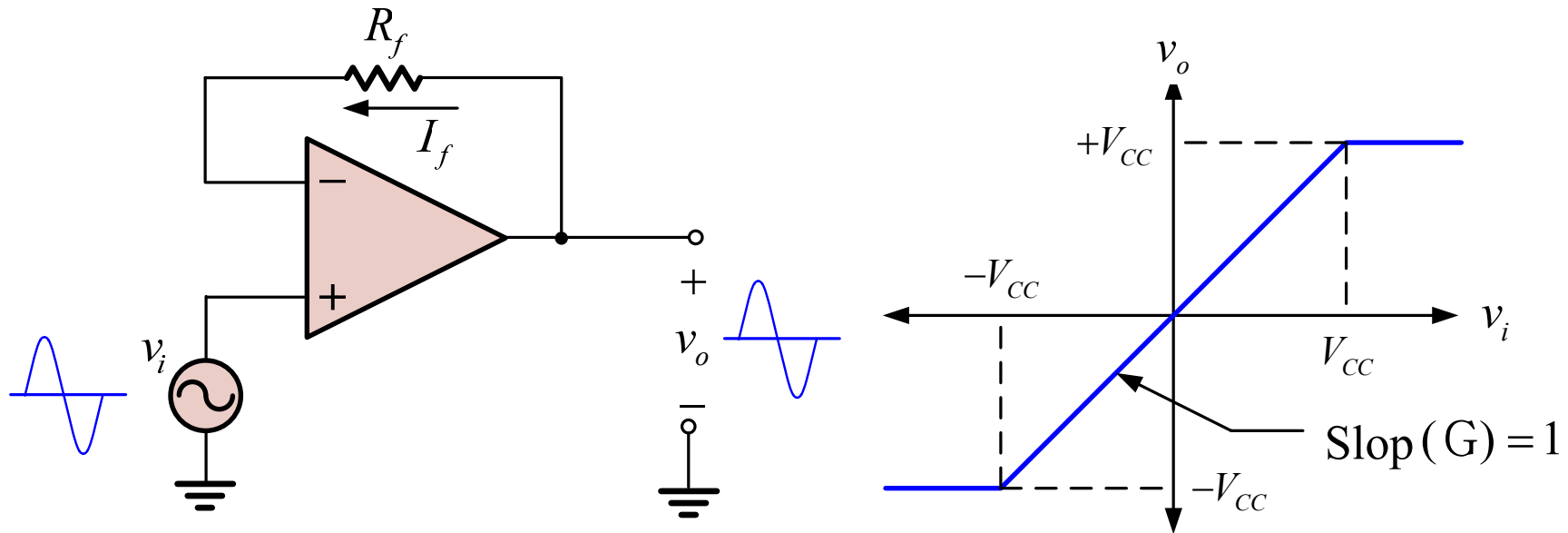

$$v_o = v_i, \quad R_{in} = \infty, \quad R_{out} = 0$$



## 2.4 Difference Amplifiers

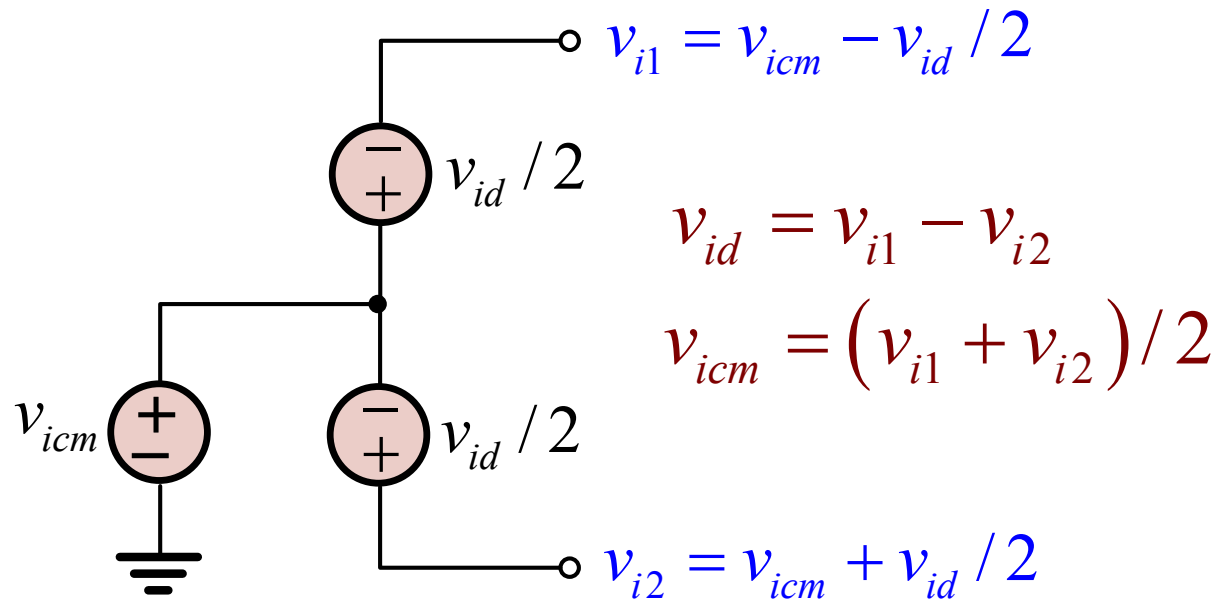


$$v_o = A_d v_{id} + A_{cm} v_{icm} = A_d v_{id} + A_d v_{id} \frac{A_{cm} v_{icm}}{A_d v_{id}}$$

$$= A_d v_{id} \left( 1 + \frac{A_{cm} v_{icm}}{A_d v_{id}} \right) = A_d v_{id} \left( 1 + \frac{1}{\text{CMRR}} \frac{v_{icm}}{v_{id}} \right)$$

$$\text{CMRR} = \frac{|A_d|}{|A_{cm}|}, \quad \text{CMRR}_{dB} = 20 \log \frac{|A_d|}{|A_{cm}|} \quad (2.14)$$


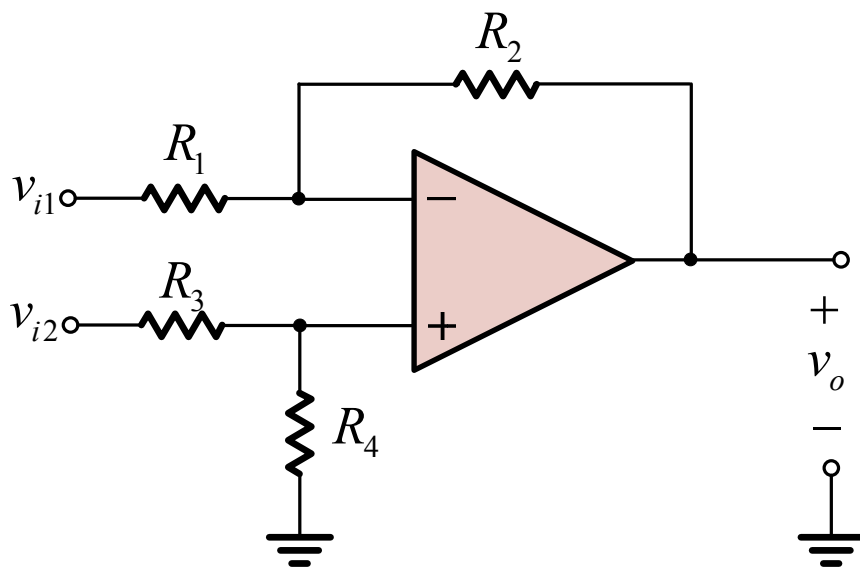
## 2.4.1 A Single Op-Amp Difference Amplifier



(1) Assume  $v_{i1} = 0$ ,

$$\begin{aligned} \text{then } v_o' &= v_+ \left( 1 + \frac{R_2}{R_1} \right) \\ &= \frac{R_4}{R_3 + R_4} v_{i2} \left( 1 + \frac{R_2}{R_1} \right) \end{aligned}$$

(2) Assume  $v_{i2} = 0$ ,

$$\text{then } v_o'' = v_{i1} \left( -\frac{R_2}{R_1} \right)$$

$$\begin{aligned} v_o &= v_o' + v_o'' \\ &= \frac{R_4}{R_3 + R_4} v_{i2} \left( 1 + \frac{R_2}{R_1} \right) + v_{i1} \left( -\frac{R_2}{R_1} \right) \end{aligned}$$

If  $R_1 = R_3 = R_a$ ,  $R_2 = R_4 = R_b$


$$\text{then } v_o = \frac{R_b}{R_a} (v_{i2} - v_{i1}) = \frac{R_b}{R_a} v_{id}$$

$$A_d = \frac{R_b}{R_a} \quad (2.17)$$





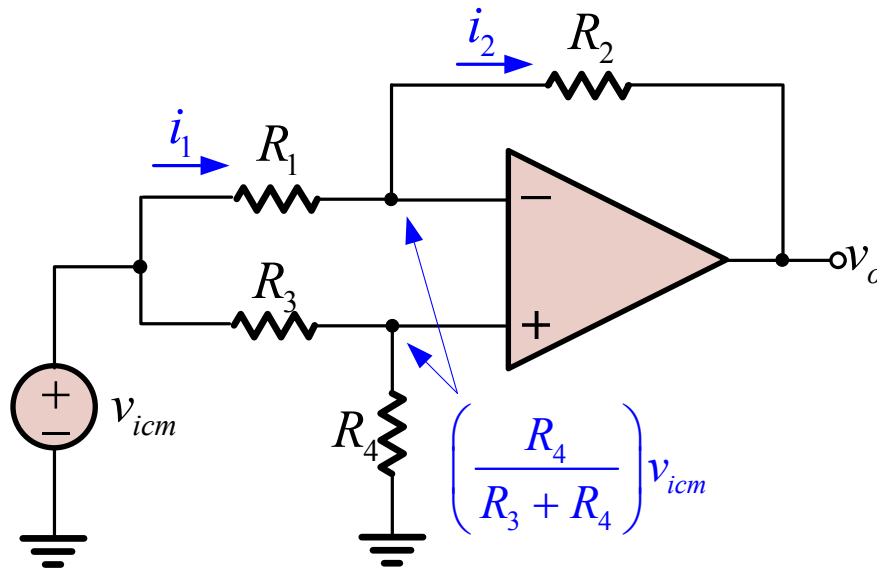A common-mode signal applied at the input



$$i_1 = i_2 = \frac{1}{R_1} \left[ v_{icm} - \frac{R_4}{R_3 + R_4} v_{icm} \right]$$

$$= \frac{1}{R_1} \frac{R_3}{R_3 + R_4} v_{icm}$$

$$v_o = v_{icm} \frac{R_4}{R_3 + R_4} - i_2 R_2$$


$$= \frac{R_4}{R_3 + R_4} v_{icm} - \frac{R_2}{R_1} \frac{R_3}{R_3 + R_4} v_{icm}$$

$$= \frac{R_4}{R_3 + R_4} \left( 1 - \frac{R_2 R_3}{R_1 R_4} \right) v_{icm}$$

$$A_{cm} = \frac{v_o}{v_{icm}} = \frac{R_4}{R_3 + R_4} \left( 1 - \frac{R_2 R_3}{R_1 R_4} \right), \quad (2.19)$$

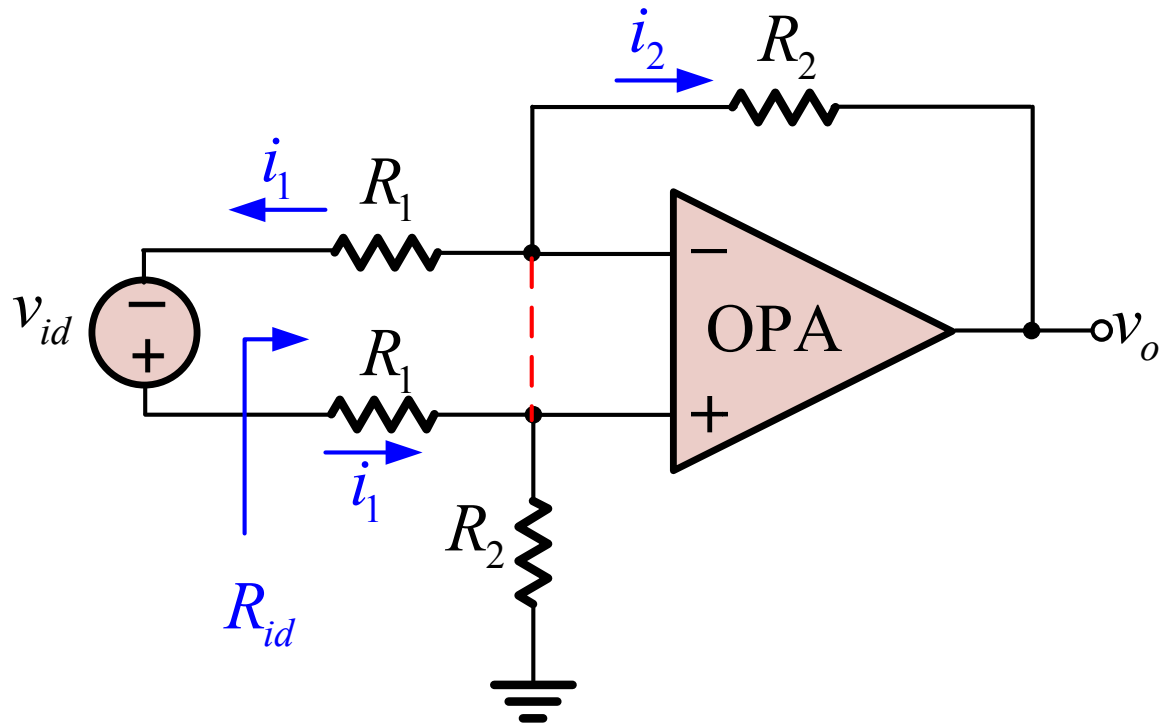If  $R_1 = R_3$ ,  $R_2 = R_4$ .  $\Rightarrow A_{cm} = 0$






$$R_{id} \equiv \frac{v_{id}}{i_i}$$

$$v_{id} = R_i i_1 + R_1 i_1$$


$$R_{id} = 2R_1 \quad (2.20)$$


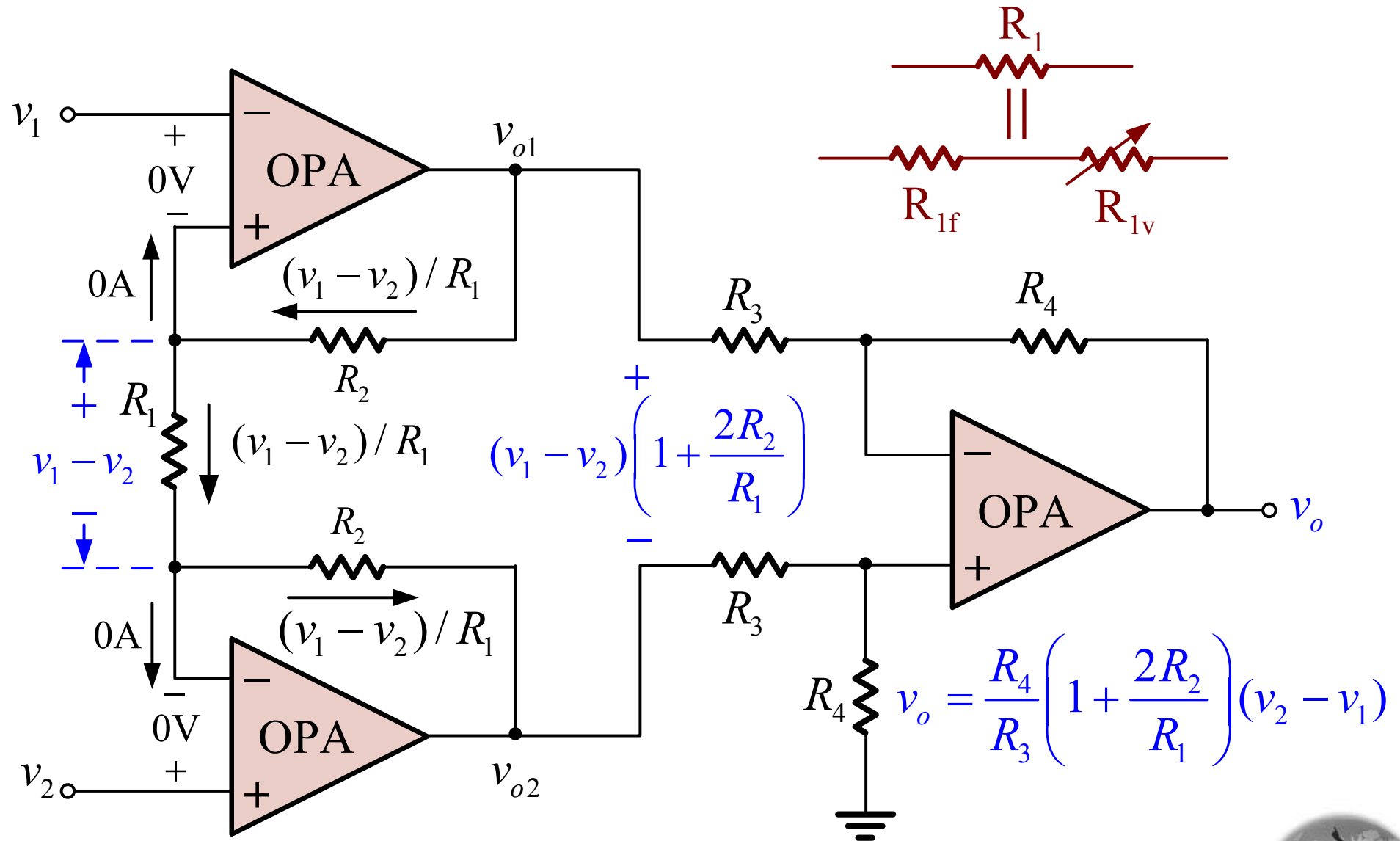
## 2.4.2 A Superior Circuit — The Instrumentation Amplifier



## 2.5 Integrators and Differentiators

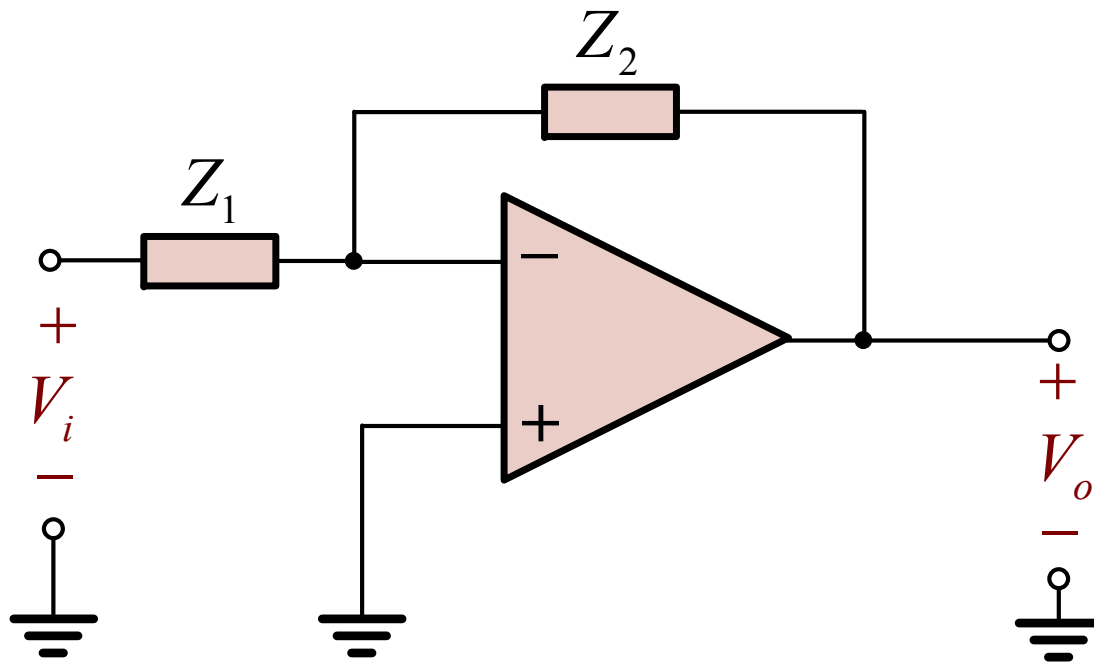


$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$$


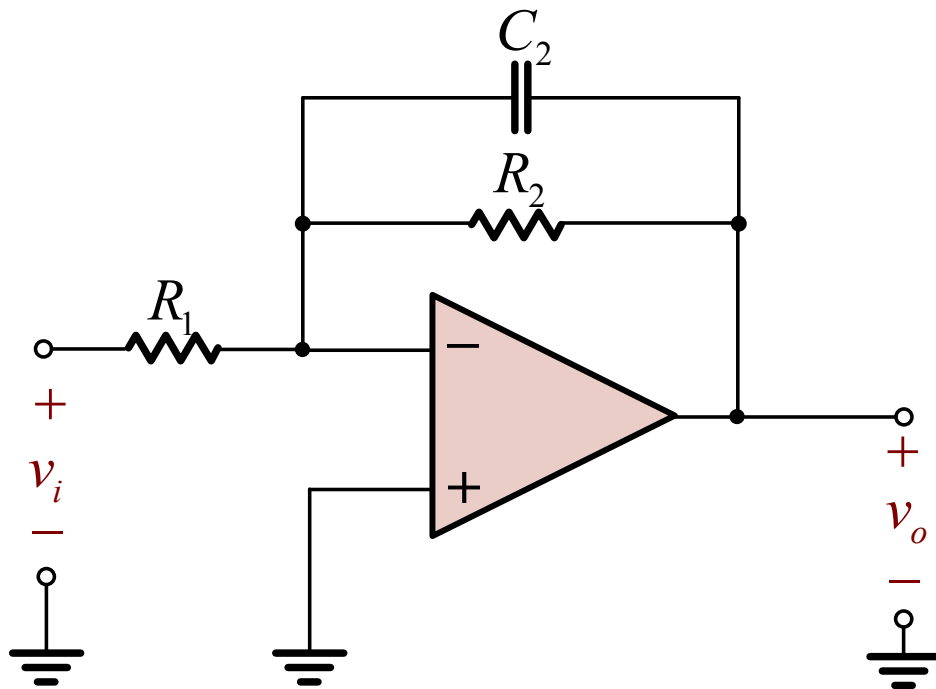
## Example 2.4

For the circuit in Fig.2.23, (a) derive the transfer function.  $v_o(s)/v_i(s)$



**Solution:**

$$\begin{aligned} \text{(a) } \frac{v_o(s)}{v_i(s)} &= -\frac{1}{z_1(s)Y_2(s)} \\ &= -\frac{1}{R_1\left(\frac{1}{R_2} + sC_2\right)} \\ &= -\frac{R_2/R_1}{1 + sC_2R_2} \end{aligned}$$

$$\omega_0 = \frac{1}{C_2R_2}$$



(b) find the dc gain

The dc gain  $K = -\frac{R_2}{R_1}$  ▲

(c) Evaluate 3-dB frequency

the 3-dB frequency  $\omega_0 = \frac{1}{C_2 R_2}$  ▲

(d) design the circuit to obtain a dc gain of 40 dB,  
a 3-dB frequency of 1 kHz, and input resistance of 1 k $\Omega$ .

**Solution:**

In order to obtain a dc gain of 40 dB, we select  $R_2/R_1 = 100$ .


For an input resistance of 1 k $\Omega$ , we select  $R_1 = 1$  k $\Omega$ , and thus

$R_2 = 100$  k $\Omega$ , for a 3-dB frequency  $f_0 = 1$  kHz, we select  $C_2$  from

$$\omega_0 = \frac{1}{C_2 R_2} \Rightarrow C_2 = \frac{1}{\omega_0 R_2} = \frac{1}{2\pi \times 1 \times 10^3 \times 100 \times 10^3} = 1.59 \text{ nF.} \quad \blacktriangle$$



## 2.5.2 Inverting Integrator

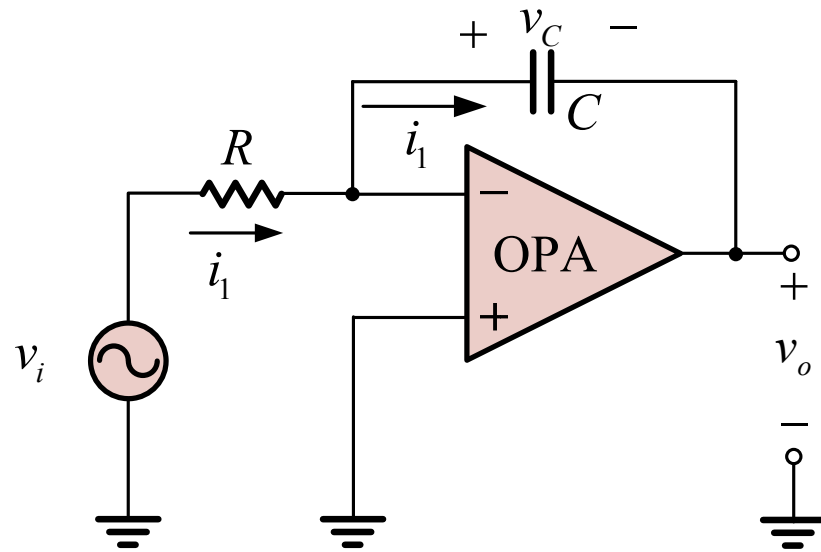


$$v_C(t) = V_C + \frac{1}{C} \int_0^t i_1(t) dt$$

$$v_o(t) = -v_C(t) = -V_C - \frac{1}{C} \int_0^t i_1(t) dt$$



We can be described alternatively in the frequency domain

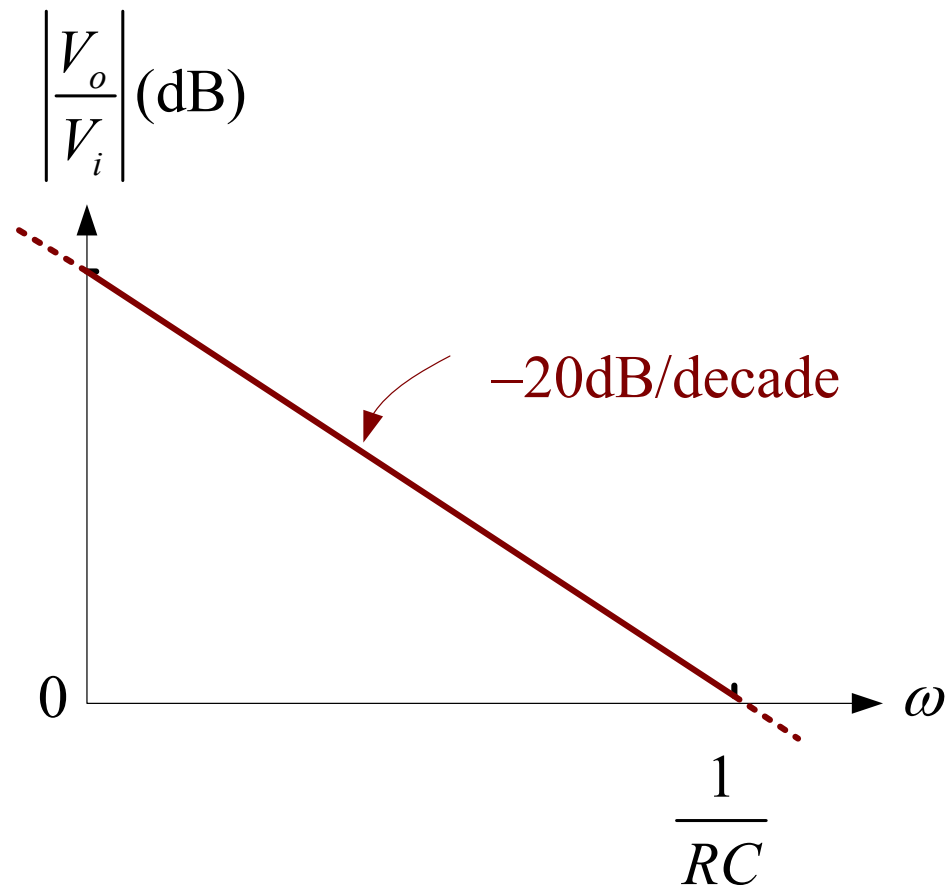by substituting  $Z_1(s) = R$ , and  $\frac{1}{Z_2(s)} = Y(s) = sC$



$$\frac{v_o(s)}{v_1(s)} = -\frac{1}{sRC}$$

$$\Rightarrow \frac{v_o(j\omega)}{v_1(j\omega)} = -\frac{1}{j\omega RC}$$


$$\left| \frac{v_o}{v_1} \right| = \frac{1}{\omega RC} = \frac{\omega_t}{\omega}, \quad \angle v_o / v_1 = 90^\circ$$

the unity gain frequency  $\omega_t$  as

$$\omega_t = \frac{1}{RC}$$





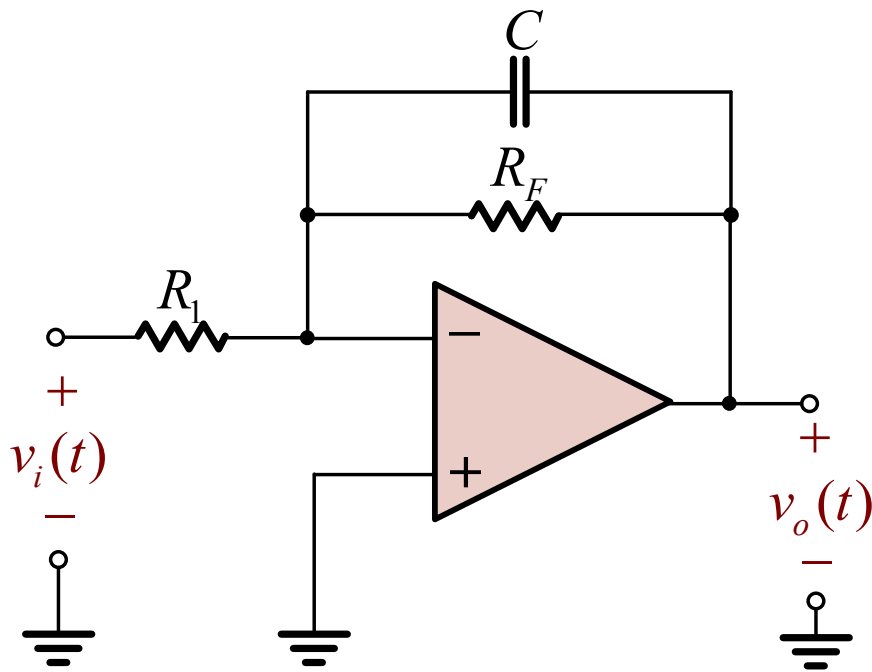

$$Z_1(s) = R$$

$$Z_2(s) = \frac{1}{\frac{1}{R_F} + sC} = \frac{R_F}{1 + sR_F C}$$

$$\frac{v_o(s)}{v_i(s)} = -\frac{R_F}{1 + sR_F C} = -\frac{R_F / R}{1 + sR_F C}$$


the Corner frequency  $\omega$  as  $\frac{1}{R_F C}$ ,

the dc gain as  $R_F / R$

Fig2.42 The Miller integrator with a large resistance  $R_F$  connected in parallel with  $C$  in order to provide negative feedback and hence finite gain at dc



## 2.5.3 The Op-Amp Differentiator

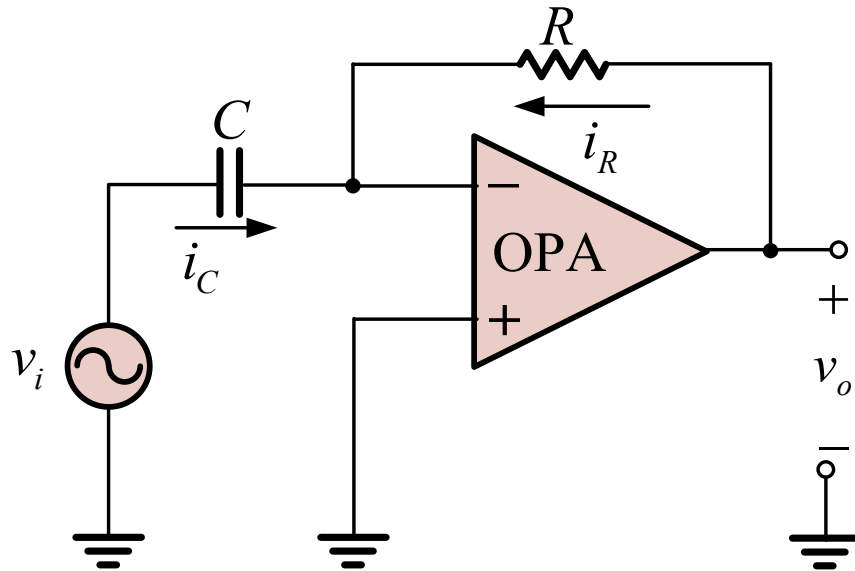


$$Q = Cv_i, \quad i_C = \frac{dQ}{dt} \Rightarrow i_C = C \frac{dv_i}{dt}, \quad I_R = \frac{v_o}{R}$$

$$-i_R = i_C \Rightarrow C \frac{dv_i}{dt} = -\frac{v_o}{R} \Rightarrow v_o = -RC \frac{dv_i}{dt}$$



The frequency domain transfer function of the differentiator circuit

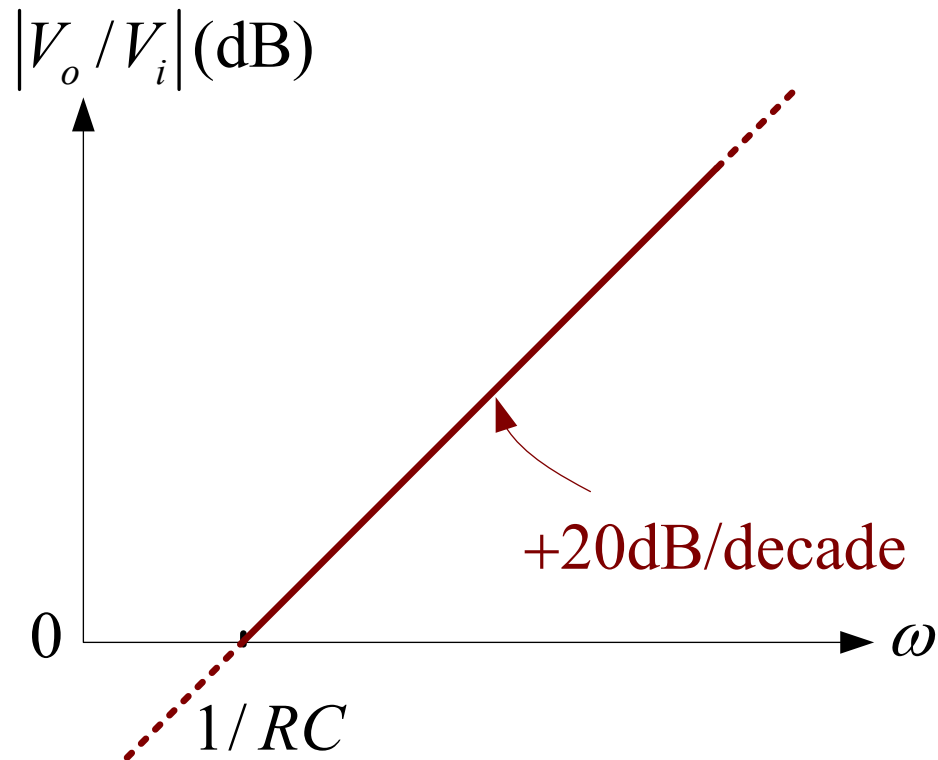can be found by substituting  $Z_1(s) = \frac{1}{sC}$ , and  $Z_2(s) = R$



$$\frac{v_o(s)}{v_1(s)} = -sRC \Rightarrow \frac{v_o(j\omega)}{v_1(j\omega)} = -j\omega RC$$

$$\left| \frac{v_o}{v_1} \right| = \omega RC = \frac{\omega}{\omega_t}$$

$$\angle v_o / v_1 = -90^\circ$$


the unity gain frequency  $\omega_t$  as

$$\omega_t = \frac{1}{RC}$$






## 2.6 DC Imperfections

### 2.6.1 Offset Voltage

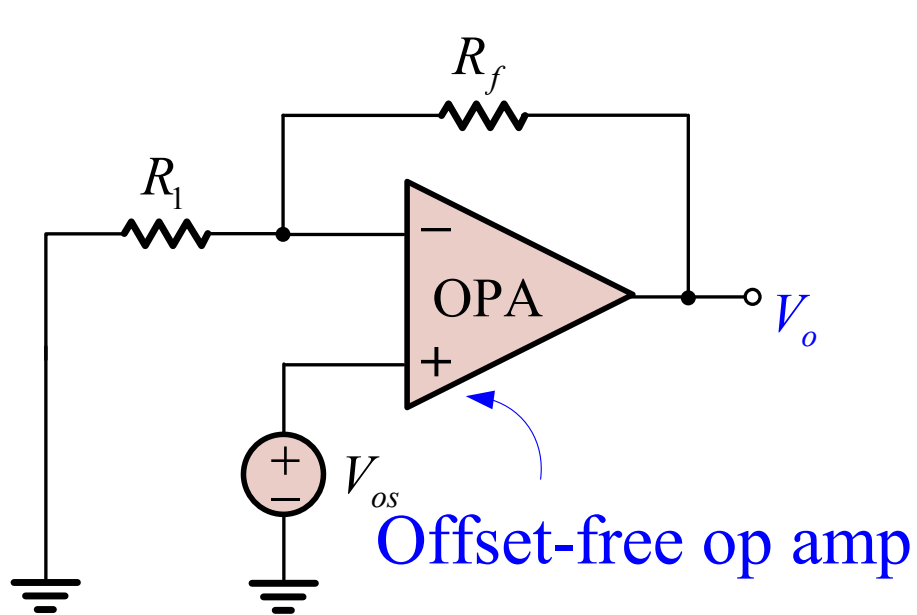

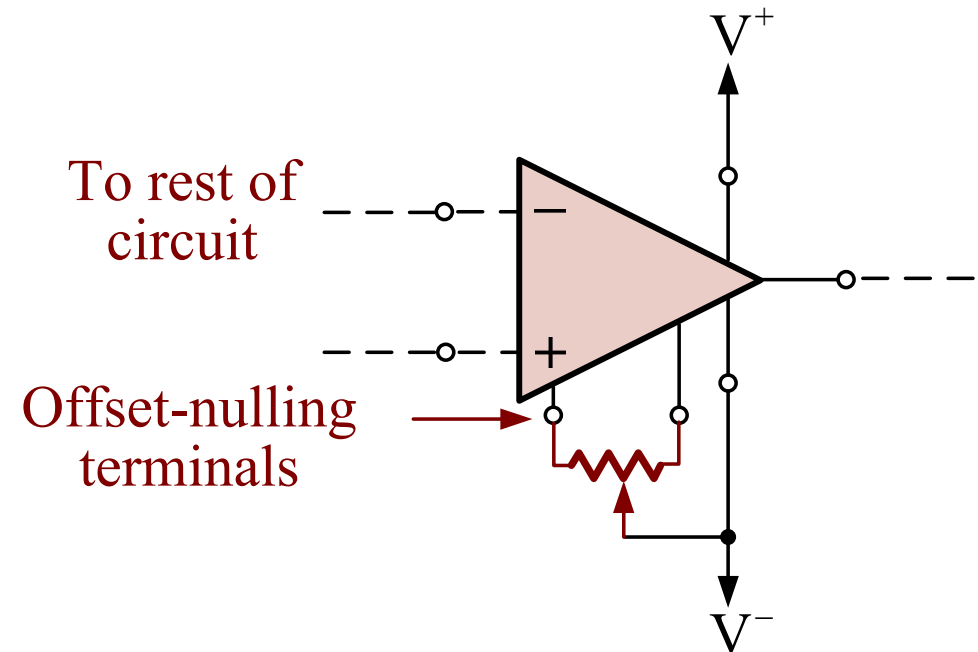
$$V_o = V_{os} \left( 1 + \frac{R_2}{R_1} \right)$$



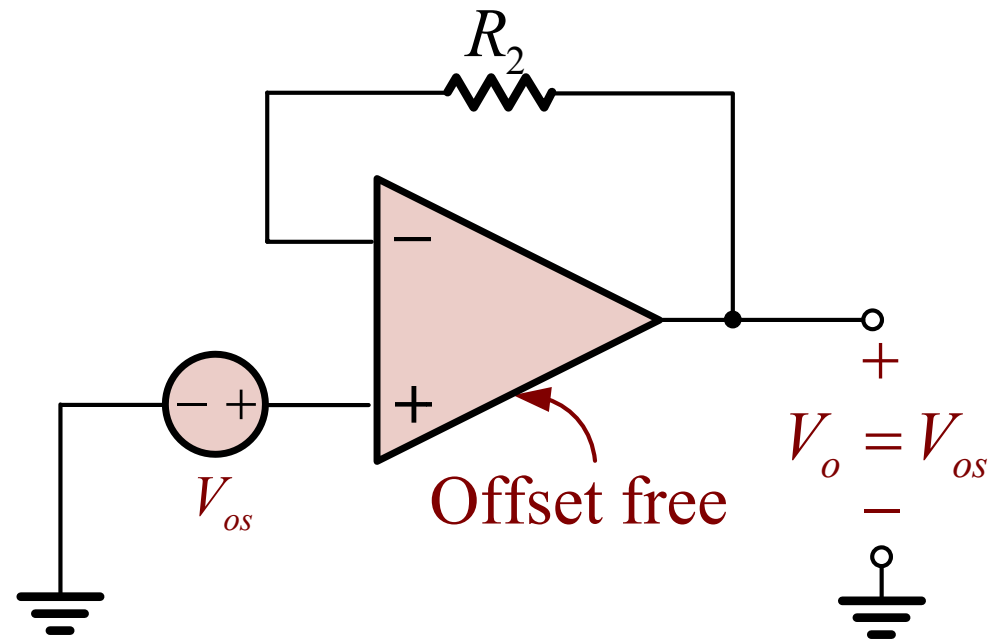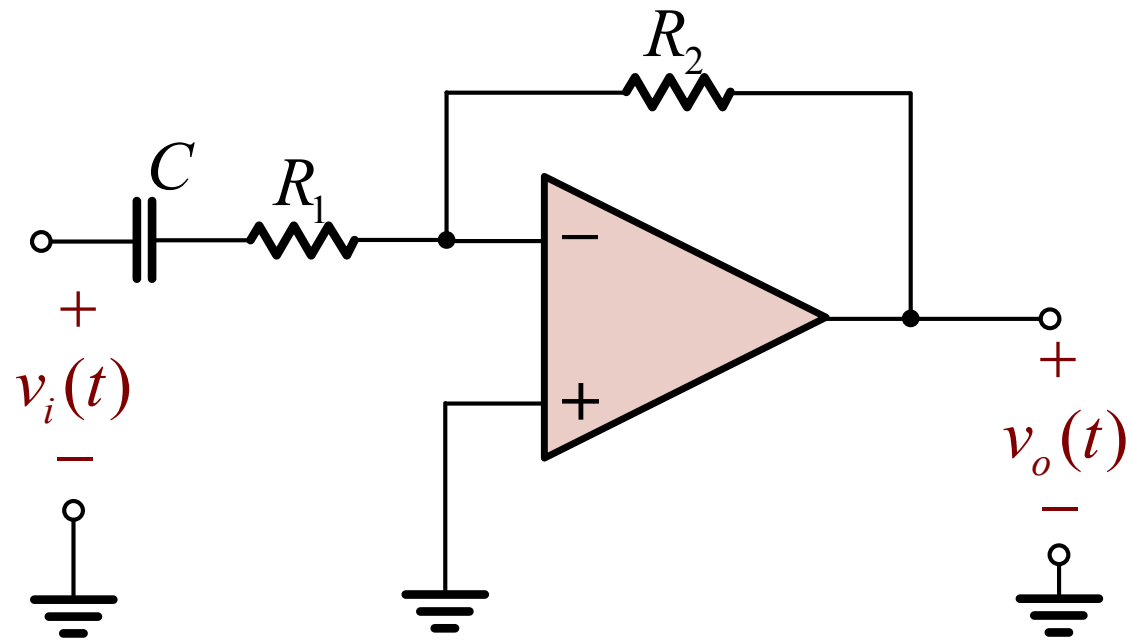


## 2.6.2 Input Bias and Offset Currents

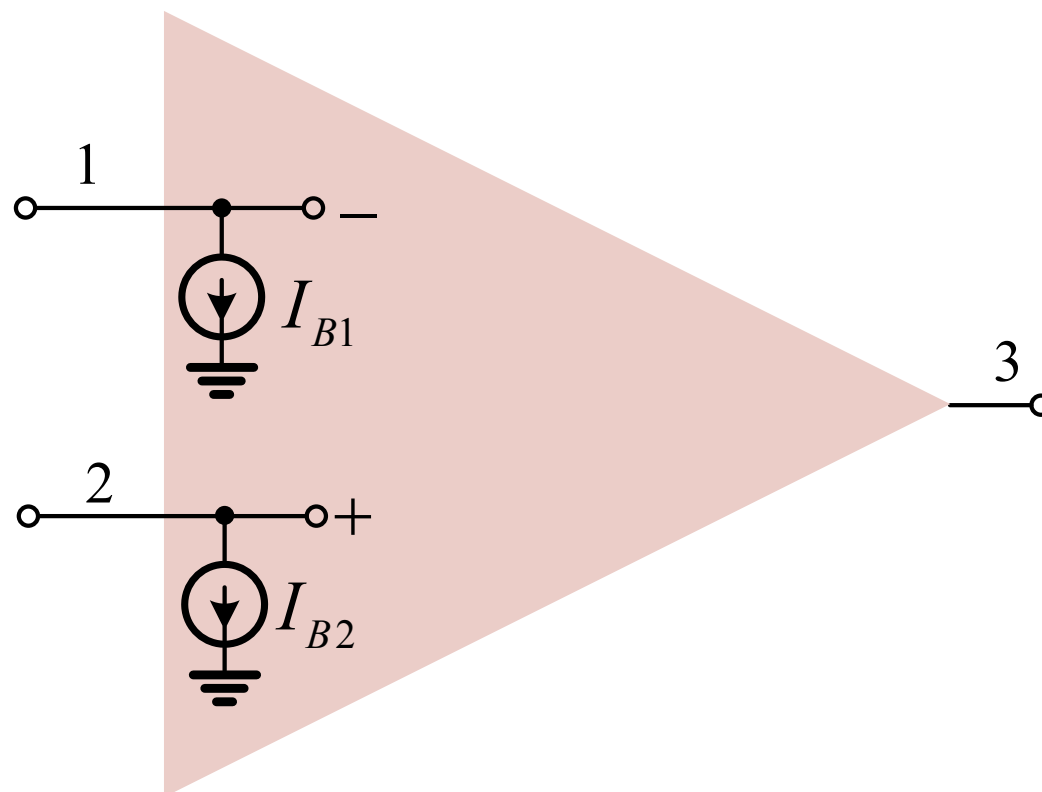

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$


$$I_{OS} = |I_{B1} - I_{B2}|$$



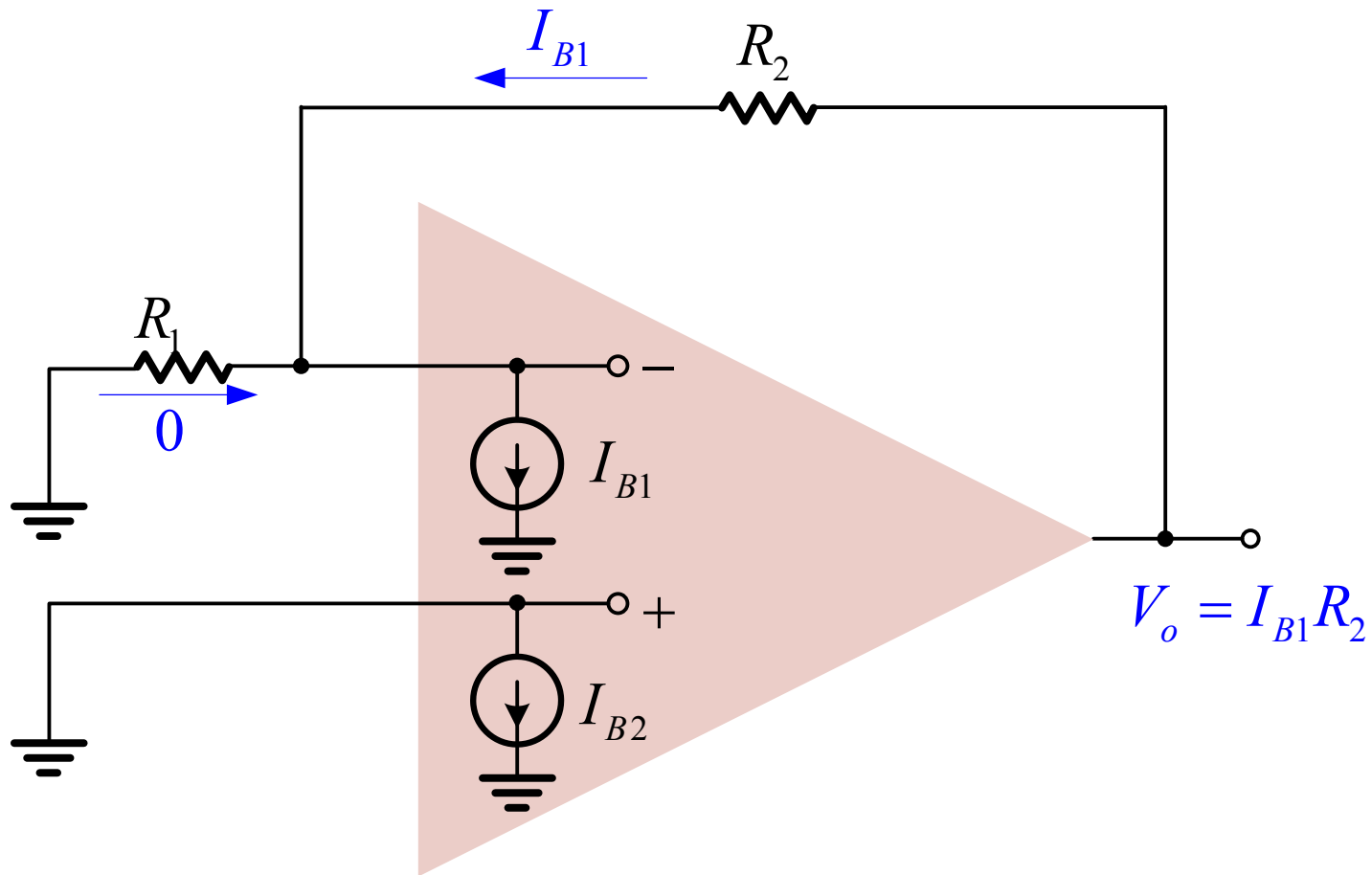

$$V_o = I_{B1} R_2 \approx I_B R_2$$



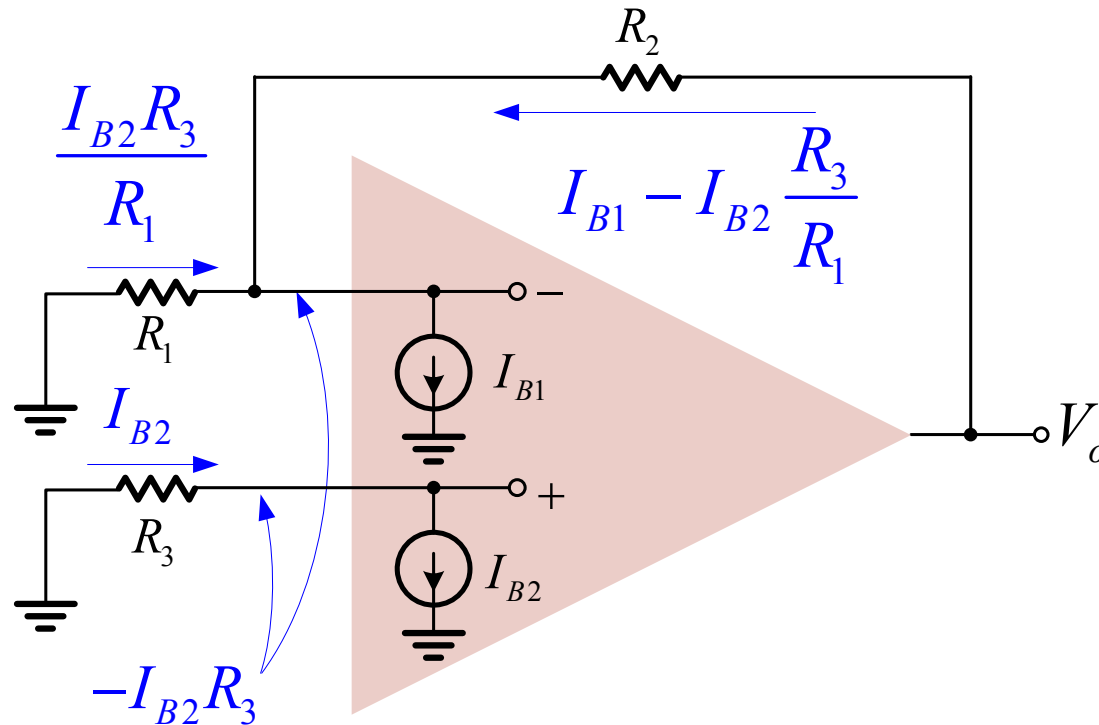

$$V_O = -I_{B2}R_3 + R_2 \left( I_{B1} - I_{B2}R_3 / R_1 \right)$$

Consider first case  $I_B = I_{B1} = I_{B2}$ , which results in

$$V_O = I_B \left[ R_2 - R_3 \left( 1 + R_2 / R_1 \right) \right]$$

Thus we can reduce  $V_O$  to zero by selecting  $R_3$  such that

$$R_3 = \frac{R_2}{\left( 1 + R_2 / R_1 \right)} = \frac{R_1 R_2}{R_1 + R_2} = R_1 // R_2$$





## 2.7 Effect of Finite Open-Loop Gain and Bandwidth on Circuit Performance

### 2.7.1 Frequency Dependence of the Open-loop Gain


$$A(s) = \frac{A_0}{1 + (s / \omega_b)} \Rightarrow A(j\omega) = \frac{A_0}{1 + (j\omega / \omega_b)} \simeq A(j\omega) = \frac{A_0 \omega_b}{j\omega}$$

$$\Rightarrow |A(j\omega)| = \frac{A_0 \omega_b}{\omega}$$

unity gain frequency  $\omega_t = A_0 \omega_b$

$$\therefore A(j\omega) = \frac{\omega_t}{j\omega} \Rightarrow |A(j\omega)| = \frac{\omega_t}{\omega} = \frac{f_t}{f}$$



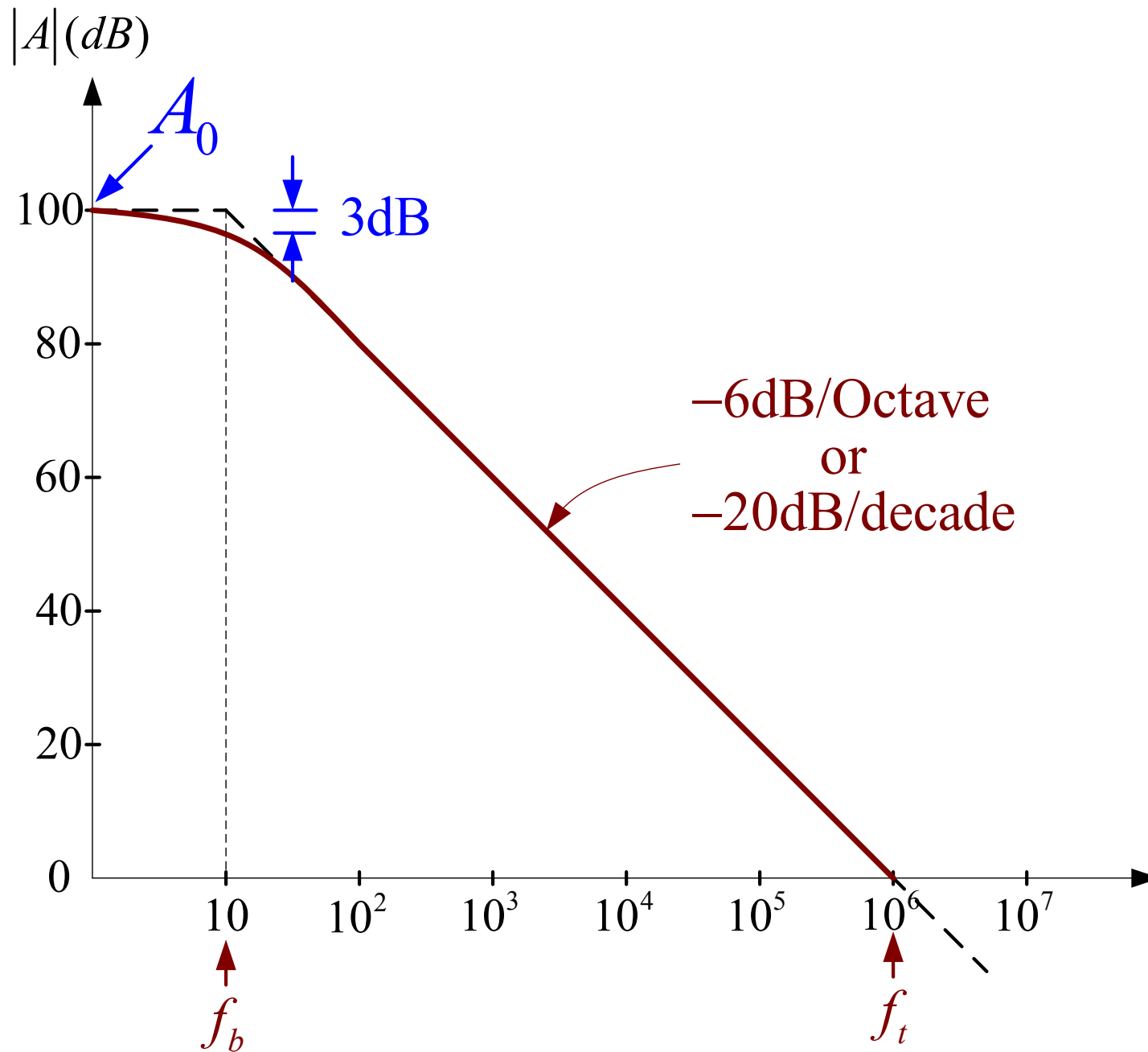

## 2.7.2 Frequency Response of Closed-loop Amplifiers

The inverting amplifier transfer function

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{-R_f / R_1}{1 + \frac{[1 + (R_f / R_1)]}{A(s)}} \Rightarrow \frac{v_o(s)}{v_i(s)} = \frac{-R_f / R_1}{1 + \frac{[1 + (R_f / R_1)]}{A_0 / [1 + (s / \omega_b)]}} \\ &= \frac{-R_f / R_1}{1 + \frac{[1 + (R_f / R_1)][1 + (s / \omega_b)]}{A_0}} \\ &= \frac{-R_f / R_1}{1 + \frac{1 + (R_f / R_1)}{A_0} + \frac{(s / \omega_b)[1 + (R_f / R_1)]}{A_0}}, \text{ where } A_0 \gg 1 + \frac{R_f}{R_1} \end{aligned}$$



$$\frac{v_o}{v_i} = \frac{-R_f / R_1}{1 + s \left( \frac{1 + (R_f / R_1)}{A_0 \omega_b} \right)} \Rightarrow \omega_{3\text{dB}} = \frac{\omega_t}{1 + (R_f / R_1)}, \quad \omega_b = \frac{\omega_t}{A_0}$$

Similarly, the noninverting amplifier transfer function:


$$\frac{v_o}{v_i} = \frac{1 + (R_f / R_1)}{1 + \frac{(1 + (R_f / R_1))}{A(s)}}$$

$$\frac{v_o(s)}{v_i(s)} = \frac{1 + (R_f / R_1)}{1 + \frac{s}{\left( \frac{\omega_t}{1 + (R_f / R_1)} \right)}} \Rightarrow \omega_{3\text{dB}} = \frac{\omega_t}{1 + (R_f / R_1)}$$



## 2.8 Large-Signal Operation of Op Amp

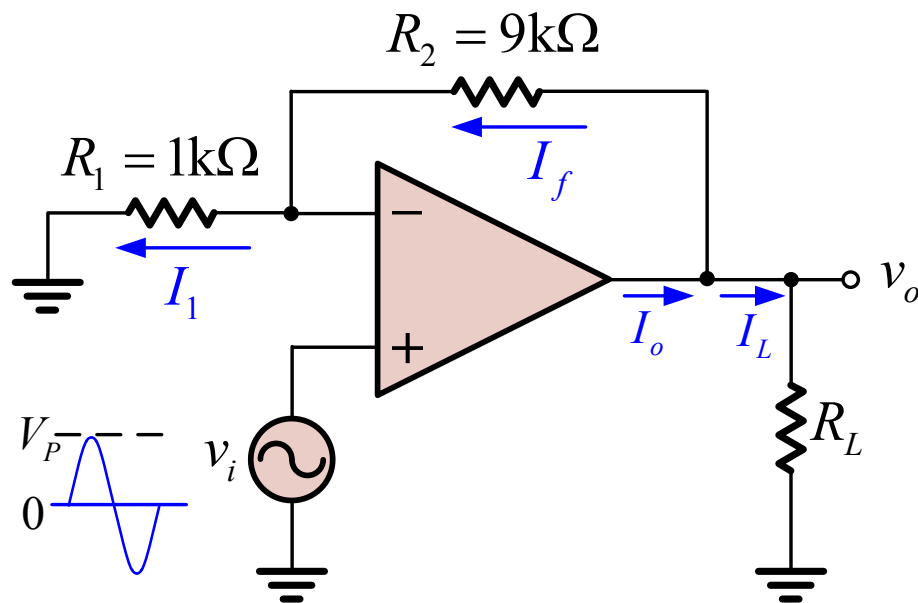**Example 2.7:** Consider the noninverting amplifier circuit shown in Fig. below. The op amp is specified to have output saturation voltages of  $\pm 13\text{V}$ , And output current limits of  $\pm 20\text{mA}$ .



(a) Find  $V_p = 1\text{V}$  and  $R_L = 1\text{k}\Omega$ , specify the signal resulting at the output of the amplifier.

Sol:

$$G = 1 + \frac{R_2}{R_1} = 10$$

$$i_L = \frac{10\text{V}}{1\text{k}\Omega} = 10\text{mA}$$

the feedback current will be

$$i_F = \frac{10\text{V}}{(9+1)\text{k}\Omega} = 1\text{mA}$$


the total output current is  $11\text{mA}$ , well under its limit of  $20\text{mA}$ .

(b) Find  $V_p=1.5V$  and  $R_L=1k\Omega$ , specify the signal resulting at the output of the amplifier.

Sol:  $V_p$  is increased to  $1.5V$ ,  $V_o$  will saturate at  $\pm 13V$

$$i_L = \frac{13V}{1k\Omega} = 13mA, \quad i_F = \frac{13V}{(9+1)k\Omega} = 1.3mA$$

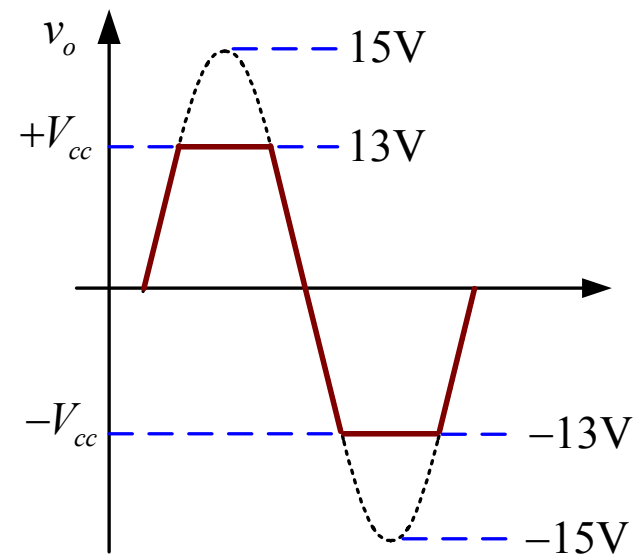$i_o = 14.3 mA$ , well under its limit of  $20 mA$ . ▲



(c) Find  $R_L=1\text{k}\Omega$ , what is the maximum value of  $V_p$  for which an undistorted sine-wave output is obtained ?

Sol: The maximum value of  $V_p$  for undistorted sine-wave output 1.3V.

The output will be a 13-V peak sine-wave.

The op-amp output current at peak will be 14.3mA.

(d) Find  $V_p=1\text{V}$ , what is the lowest value of  $R_L$  for which an undistorted sine-wave output is obtained ?


Sol:  $V_p = 1.5\text{V}$ ,

$$i_{o(\text{max})} = 20\text{mA} = \frac{10\text{V}}{R_{L\text{min}}} + \frac{10\text{V}}{9\text{k}\Omega + 1\text{k}\Omega}$$

$$R_{L\text{min}} = 526\Omega.$$






## 2.8.3 Slew Rate

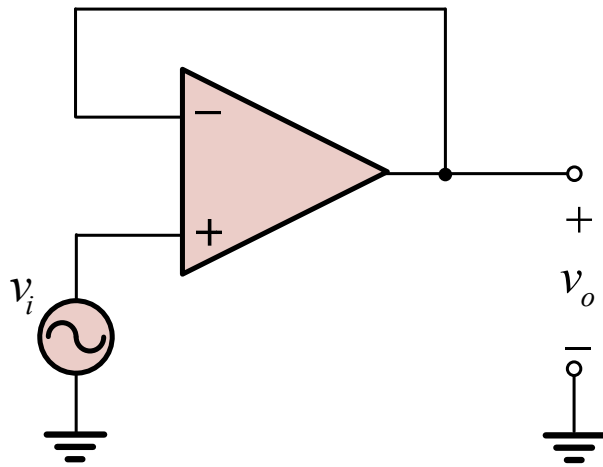

$$SR = \left. \frac{dv_o}{dt} \right|_{\max}$$

$$\frac{v_o}{v_i} = \frac{1}{1 + s/\omega_t}$$

$$v_o(t) = V(1 - e^{-\omega_t t})$$

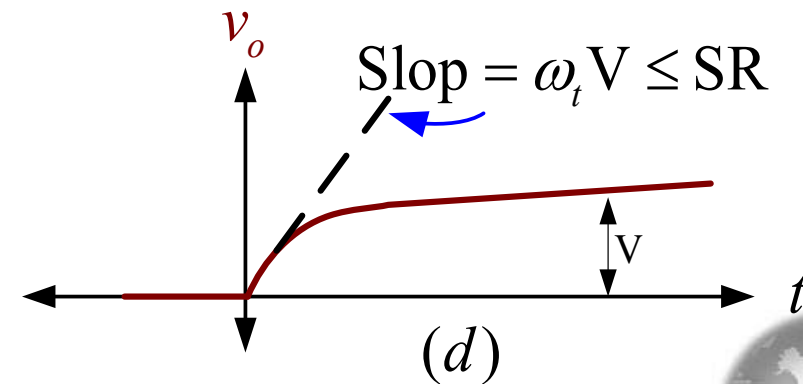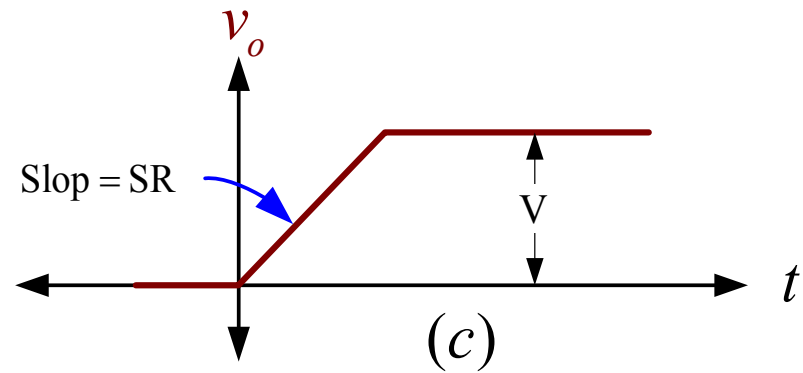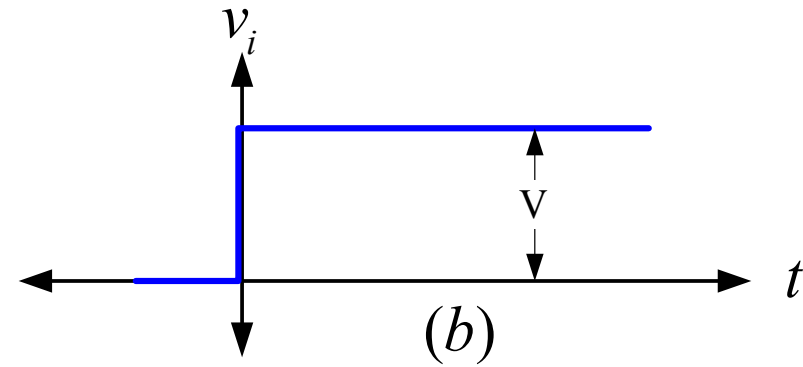




## 2.8.4 Full-Power Bandwidth

$$v_i = \hat{V}_i \sin \omega t$$

$$\frac{dv_i}{dt} = \omega \hat{V}_i \cos \omega t$$

$$SR = \omega_M V_{o_{\max}}$$

$$f_M = \frac{SR}{2\pi V_{o_{\max}}}$$

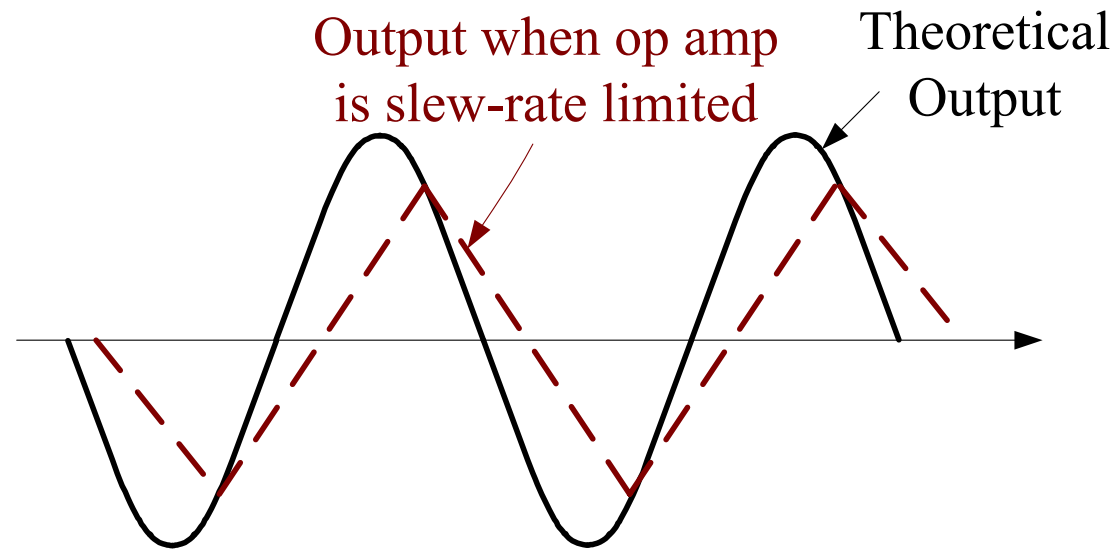

The Maximum amplitude of the undistorted output sinusoid is given by

$$V_o = V_{o_{\max}} \left( \frac{\omega_M}{\omega} \right)$$



# Thanks For Your Attention !

---

## Q&A

